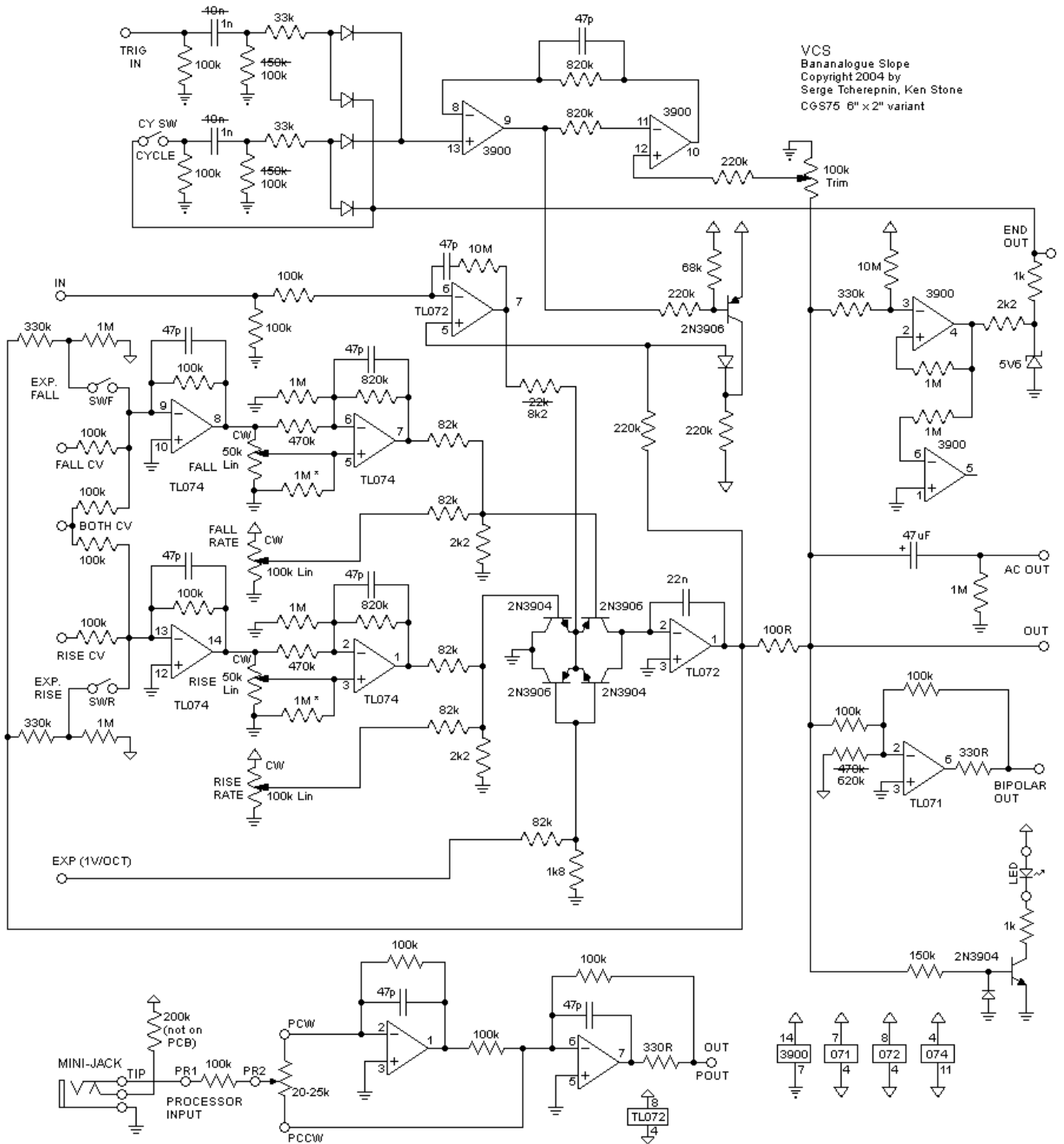



The schematic for the Euro version is different in the area of the switches SWF and SWR, though functionality remains the same.

For those interested in the theory of operation, I recommend [Tim Stinchcombe's page on the subject](#).



The schematic of the VCS. Several suggested component changes are indicated on the diagram.

Construction

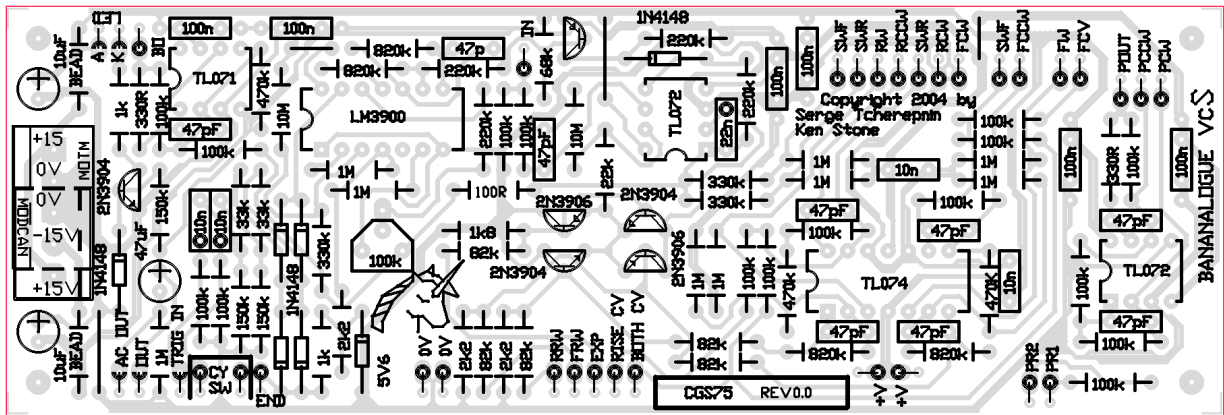

The component overlay for the VCS. [Click here for an enlarged, printable version. Print at 300dpi for a correct scale printout.](#)

Notes: The CGS75 version of the PCB includes a voltage processor. This allows a signal to be swept from $_1$ gain to -1 gain (i.e. inverted). It can be used with the "both" input or signal input, or it can be ignored and the associated parts left of the PCB.

It is a good idea to match the transistors of the same type in the core with each other. At least use transistors from the same batch.

On the first run of these PCBs (REV0.0 red boards) the specified 220k resistor connected to the emitters of the four transistors should be 8k2. On the VER1.0 boards, the 22k resistor in this location should be 8k2.

Before you start assembly, check the board for etching faults. Look for any shorts between tracks, or open circuits due to over etching. Take this opportunity to sand the edges of the board if needed, removing any splinters or rough edges. (With the boards supplied by me, the edges are already milled, and etching faults are very rare.)

When you are happy with the printed circuit board, construction can proceed as normal, starting with the resistors first, followed by the IC socket if used, then moving onto the taller components.

Take particular care with the orientation of the polarized components such as electrolytics, diodes, transistors and ICs.

When inserting ICs into sockets, take care not to accidentally bend any of the pins under the chip. Also, make sure the notch on the chip is aligned with the notch marked on the PCB overlay.

The holes without pads near the input and output pads are to allow a wire to be fed up from the bottom side, looped over and then soldered to the pad. The slack is then pulled back through the hole, creating an anchor that holds the wire by its insulation, reducing the chance of wire breakage. It is also helpful for a system such as Serge, where wires are traditionally connected from the solder side of the PCB.

A problem in the genuine Serge is that cycle locks up at various frequencies due to a charge imbalance in the trigger circuit. If you experience this problem, it can be solved by changing the 10n capacitor to 1n. These changes are marked on the circuit diagram.

ac out	ac out jack
bo	bi-polar output jack
out	out jack
trig in	trigger in jack
cy sw	(x 2) cycle switch. Switch connects these together for cycle mode
end	end out jack
rrw	rise rate wiper
	CW end of rise rate pot connects to +ve
	CCW end of rise rate pot connects to 0V
frw	fall rate wiper
	CW end of fall rate pot connects to +ve
	CCW end of fall rate pot connects to 0V
exp	exponential cv jack
rise cv	rise cv jack
both cv	both cv jack
in	input jack
swf	(x 2) fall switch. Switch connects these together for exp. response.
swr	(x 2) rise switch, Switch connects these together for exp. response.
rw	rise pot wiper
rccw	rise pot counter-clockwise
rcw	rise pot clockwise
fcw	fall pot clockwise
fccw	fall pot counter-clockwise

fw	fall pot wiper
fcv	fall cv jack
pout	processor output jack
pccw	processor pot ccw
pcw	processor pot cw
pr1	processor input
pr2	processor pot wiper

Note: You may need to reverse the connections to some of the pots to get them to work in the direction you wish.

Setting up

Adjustments on the VCS board are set to obtain a 0 to +5 volt level when the unit is cycling, producing a 100Hz triangle wave. An oscilloscope is required for this adjustment. In an oscilloscope is not available, adjust for the least distorted sounding waveshape.

Notes:

- **PCB info:** 2" x 6" with four 3mm mounting holes 0.15" in from the edges.
- Will run on +/- 12 volts or +/-15 volts.
- Please [email me](#) if you find any errors.

Parts list

This is a guide only. Parts needed will vary with individual constructor's needs.

Classic Serge style knobs can be purchased from

[Small Bear Electronics LLC](#)

[phenolic clone of Davies 1900H](#)

[ABS clone of Davies 1900H](#)

[Colored ABS clones of Davies 1900H](#)

If anyone is interested in buying these boards, please check the [PCBs for Sale](#) page to see if I have any in stock.

Can't find the parts? See the [parts FAQ](#) to see if I've already answered the question. Also see the [CGS Synth discussion group](#).

Part	Quantity
Capacitors	
47pF	9
1n	2
10n	2
22n	1
100n	6
10uF 25V	2
47uF 25V	1
Resistors	
100R	1
330R	2
1k	2
1k8	1
2k2	3
8k2	1
33k	2
68k	1
82k	5
100k	18
150k	1
200k	1
220k	4
330k	3
470k	2
600k	1
820k	4
1M	9
10M	2
100k trimmer	1
50k lin pot	2
20k lin pot	1
100k lin pot	2
Semi's	
LED	1
1N4148	6
2N3904	3
2N3906	3
5V6 400mW Zener	1
TL071	1
TL072	2
TL074	1
LM3900	1
Misc.	
Ferrite Bead	2
SPST switch	3

0.156 4 pin connector	1
CGS75 PCB	1

Article, art & design copyright 2006 by [Ken Stone](#)

[Modular Synth Home](#)

[Disclaimer](#)