


Ring Modulator

for music synthesizers.

This module is a variation on the 1973 Classic Serge R6 Ring Modulator.


From the catalog (abridged): The RING MODULATOR (MOD) is an AC or DC coupled Ring Modulator featuring superior audio processing capabilities. The Ring Modulator offers two VC inputs in addition to the two signal inputs which may be used to perform voltage controlled transitions between full ring modulation and amplitude modulation.

A little on how it works:

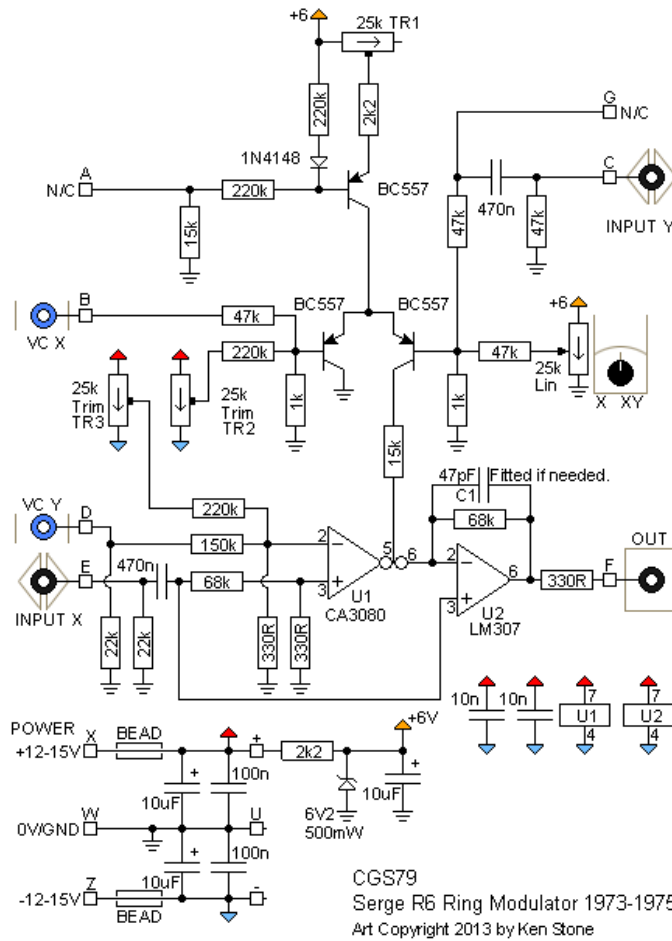


The schematic of the Ring Modulator module.

Construction

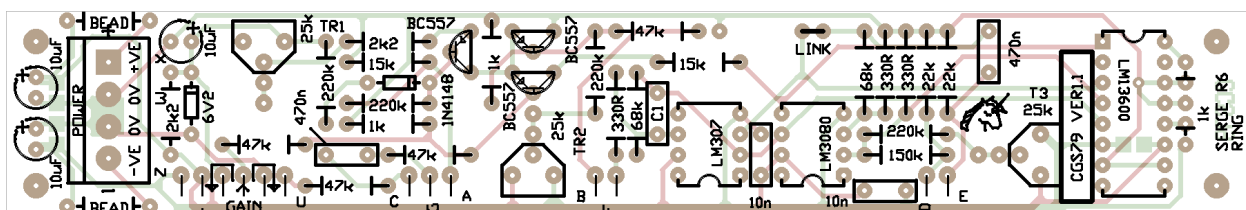

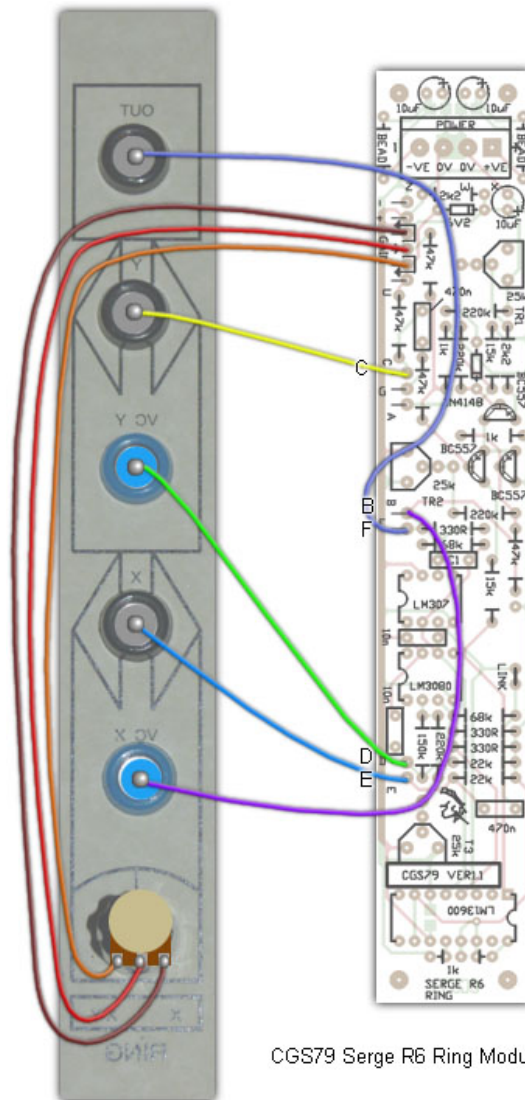The component overlay for the VER1.1 PCB. On the VER1.0 PCB the 22k resistor nearest to the power connector should be a 2k2, as shown above (next to "W"). [Click here for an enlarged, printable version.](http://www.cgs.synth.net:80/modules/cgs79_ring.html) [Print at 300dpi.](http://www.cgs.synth.net:80/modules/cgs79_ring.html)



CGS79 Serge R6 Ring Modulator

The wiring required to use the PCB as a Ring Modulator.

Set Up

Suggested setup procedure:

Preliminary adjustments -


Adjust the panel potentiometer all the way to ground (CW).

Adjust TR3 to center position

Adjust TR2 fully to +V position

Input 500 Hz 0/5V sawtooth into Input X AND pad A (no panel connection)

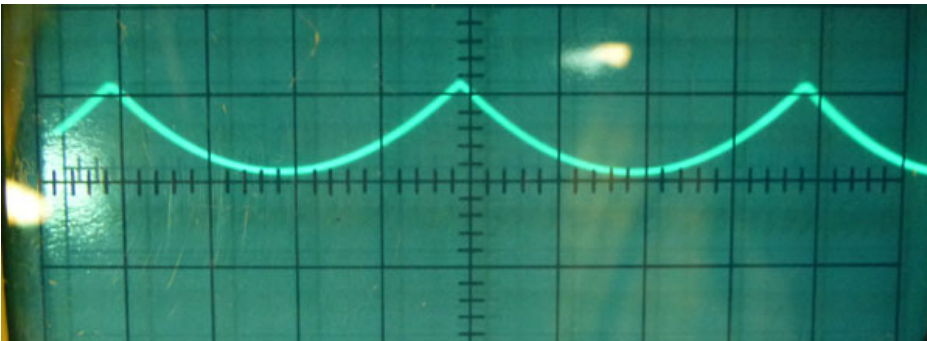While looking at the output, adjust TR1 until the output waveform is perfectly symmetrical (and rectified), as below.



Note that the rectified sawtooth wave has a distinctly rounded bottom.

Now disconnect the sawtooth from Input X (keeping it connected to pad A).

Turn the scope sensitivity up. Adjust TR3 until the least feed through of the sawtooth is seen (or heard).

It would be good to repeat the initial adjustment of TR1 as above, now that TR3 has been set.

Finally, with the sawtooth still connected to Input X, connect it to Input Y.

Now adjust TR2 to achieve as symmetrical an output at 1000 Hz as possible. Note that the waveform will be somewhat different to the previous one, due to the non linear characteristic of the transistor pair.

Alternative method:

Set X-XY pot to X (CCW).

Connect an audio frequency triangle wave to X input.

Adjust trimmers TR2 and TR3 for minimum breakthrough. This will require alternately adjusting the two trimmers until you get the desired result.

Move the audio frequency triangle wave to the Y input.

Connect a second triangle wave, this time at around 1Hz, to the X input.

Adjust TR1 for a balanced "throb".

For those interested, original Serge kit assembly and set-up instructions can be found here:

[Ring Modulator](#)

Info on the original Serge module can be found here:

[Ring Modulator](#)

Notes:

- 330R refers to 330 ohms. 100n = 0.1 uF.
- The module will work on +/-12 volts or +/-15 volts.
- **PCB info:** 6" x 1" with 3mm mounting holes 0.15" in from the edges.
- Please [e-mail me](#) if you find any errors.

Parts list

This is a guide only. Parts needed will vary with individual constructor's needs.

If anyone is interested in buying these boards, please check the [PCBs for Sale](#) page to see if I have any in stock.

Can't find the parts? See the [parts FAQ](#) to see if I've already answered the question. Also see the [CGS Synth discussion group](#).

Resistors (1% metal film)	
330Ω	3
1k	3
2k2	2
15k	2
22k	4
25k trimmer	3
25k lin pot	1
33k	1
47k	2
68k	2
220k	4
Capacitors	
100nF 1206 SMT (=0.1uF) see text.	3
10nF (=0.01uF)	2
470nF (=0.47uF)	2
10uF electrolytic	3
Semi's	
1N4148	1
6V2	1
BC557	3
LM307	1
LM3080	1
LM13600	See text
Misc.	
Ferrite Bead	2
MTA-156 header 4Pin	1
CGS79 PCB	1

Article, art & design copyright 2013 by [Ken Stone](#)

[Modular Synth Home](#)

[Disclaimer](#)

